



VLSILAB  
REPORT

2024

(CO3098) LSI logic design  
Floating-point ALU Specification

**Submitted to: Mr. Huynh Phuc Nghi**

**Submitted by: To Hoang Phong - 2112012**  
**Vu Huynh Tan Phat - 2114391**

**Ho Chi Minh University of Technology (HCMUT)**  
**The faculty of Computer Science and Engineering**

Author	Group 1
Date	2024/04/08
Version	1

## Contents

<a href="#">1 Interface</a>	<a href="#">3</a>
<a href="#">2 Functional implementation</a>	<a href="#">4</a>
<a href="#">3 Diagram</a>	<a href="#">5</a>
<a href="#">4 Appendix</a>	<a href="#">5</a>

## 1 Interface

 


Figure 1: The figure of floating-point ALU System

signal	Width	In/Out	Description
para1	32	Input	The first parameter for the calculation that is presented in the single precision floating point form (a 32-bit approximation of a real number)
para2	32	Input	The second parameter for the calculation that is presented in the single precision floating point form
alu_op	2	Input	The signal for choosing operators in ALU. The next section will describe this signal in detail
out	32	Output	The result of calculation processes that is presented in the single precision floating point form
zero	1	Output	The signal for users to notice whether all bits in the result is 0 or not
under_overflow	1	Output	The signal for users to notice underflow or overflow cases

Table 1: Descriptions of signals in floating-point ALU

## 2 Functional implementation

- A float-point arithmetic logic unit system that is the operation of two single precision floating point numbers.
- For more details in single precision floating point numbers, please read the [Appendix](#).
- System's operation based on three input signals
  - para1
  - para2
  - alu\_op
- The system specification
  - para1, para2 are 32-bit floating point numbers
  - The operator will be decided by **alu\_op** signal
    - alu\_op = 00<sub>b</sub>: out = para1 + para2 (the addition operator)
    - alu\_op = 01<sub>b</sub>: out = para1 - para2 (the subtraction operator)
    - alu\_op = 10<sub>b</sub>: out = para1 \* para2 (the multiplication operator)
    - Others: out = 0
  - The system can handle all floating point numbers, except for infinity, NA (not-a-number) and denormalized number cases
- zero = 1 when out = 0000<sub>h</sub> (0 value in the floating point number set)
- Underflow or overflow cases:
  - In underflow cases
    - The out signal will equal to FF800000<sub>h</sub> ( $-\infty$ ) and under\_overflow = 1
  - In overflow cases
    - The out signal will equal to 7F800000<sub>h</sub> ( $+\infty$ ) and under\_overflow = 1
  - **In multiplication operators**
    - Overflow or underflow cases are defined in exponent parts, disregard for the sign part.
    - E.g: Overflow case:  $-2^{120} * 2^{120} = -2^{240}$ , the absolute value is greater than the maximum number.
    - Underflow case:  $2^{-120} * 2^{-120} = 2^{-240}$ , the absolute value is less than the minimum positive number.
    - The output value in over/underflow cases is same as the above rule.

### 3 Diagram

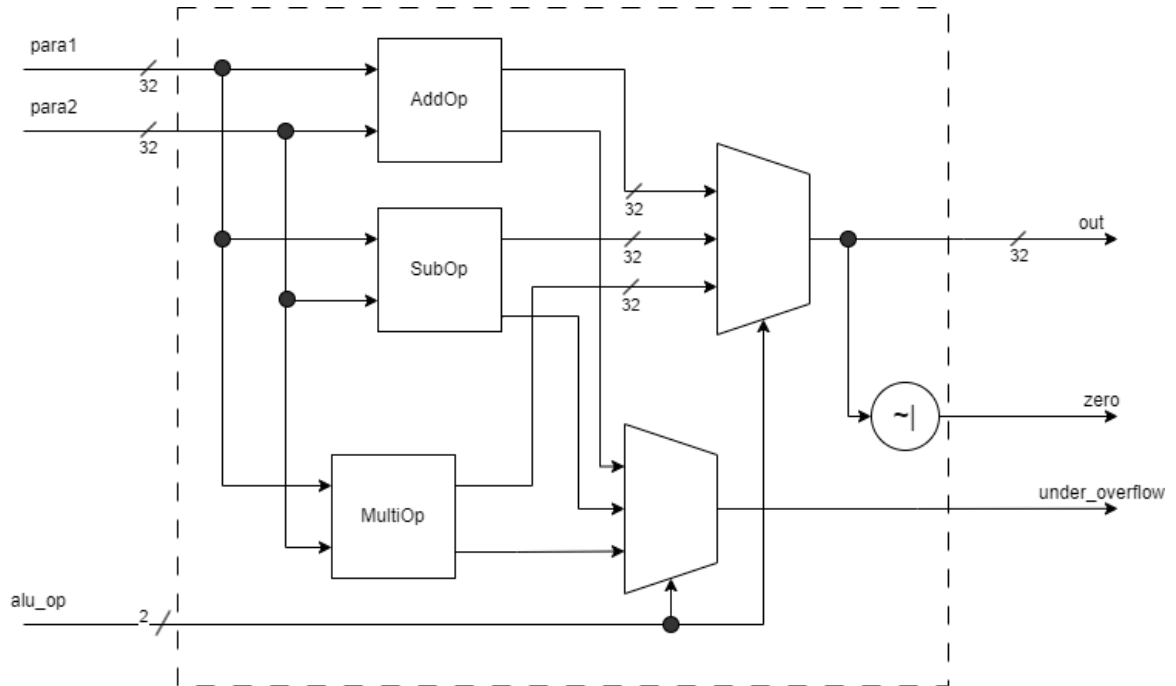


Figure 2: The system diagram

#### Details

Sub-modules	Interface	Descriptions
<b>AddOp</b>	input [31:0] para1 input [31:0] para2 output [31:0] out output under_overflow	The sub-module handles addition operators between two 32-bit inputs. There is an under_overflow signal for verify underflow or overflow cases
<b>SubOp</b>	input [31:0] para1 input [31:0] para2 output [31:0] out output under_overflow	The sub-module handles subtraction operators between two 32-bit inputs. There is an under_overflow signal for verify underflow or overflow cases
<b>MultiOp</b>	input [31:0] para1 input [31:0] para2 output [31:0] out output under_overflow	The sub-module handles multiplication operators between two 32-bit inputs. There is an under_overflow signal for verify underflow or overflow cases
<b>~ </b>	input [31:0] number output zero	The sub-module is a reduction 'nor' operator that help to notice whether bits of number are all 0

Table 2: Descriptions of sub-modules in floating-point ALU

### 4 Appendix

Reference: David A.Patterson & John L. Hennessy, *Computer Organization and Design RISC-V edition*

#### Single precision floating point numbers

Floating-point numbers are usually a multiple of the size of a word. The representation of a RISC-V floating-point number is shown below, where s is the

sign of the floating-point number (1 meaning negative), exponent is the value of the 8-bit exponent field (including the sign of the exponent), and fraction is the 23-bit number.



Figure 3: The number format

In general, floating-point numbers are of the form:

$$(-1)^S * F * 2^E \quad (1)$$

F involves the value in the fraction field and E involves the value in the exponent field. However, to pack even more bits into the number, IEEE 754 makes the leading 1 bit of normalized binary numbers implicit. Hence, the number is actually 24 bits long in single precision (implied 1 and a 23-bit fraction).

$$(-1)^S * (1 + Fraction) * 2^E \quad (2)$$

where the bits of the fraction represent a number between 0 and 1 and E specifies the value in the exponent field, to be given in detail shortly. If we number the bits of the fraction from left to right f<sub>1</sub>, f<sub>2</sub>, f<sub>3</sub>, ..., then the value is

$$(-1)^S * (1 + f_1 * 2^{-1} + f_2 * 2^{-2} + f_3 * 2^{-3} + ...) * 2^E \quad (3)$$

Single precision		Object represented
Exponent	Fraction	
0	0	0
0	Nonzero	± denormalized number
1–254	Anything	± floating-point number
255	0	± infinity
255	Nonzero	NaN (Not a Number)

Figure 4: IEEE754 number encoder

IEEE 754 uses a bias of 127 for single precision, so an exponent of -1 is represented by the bit pattern of the value  $-1 + 127_d$ , or  $126_d = 01111110_b$ , and +1 is represented by  $1 + 127$ , or  $128_d = 10000000_b$ . Biased exponent means that

the value represented by a floating-point number is really:

$$(-1)^S * (1 + Fraction) * 2^{E-127} \quad (4)$$

The minimum positive number is  $2^{-126}$

The maximum positive number is  $(2 - 2^{-23}) * 2^{127}$

### Addition and subtraction operators

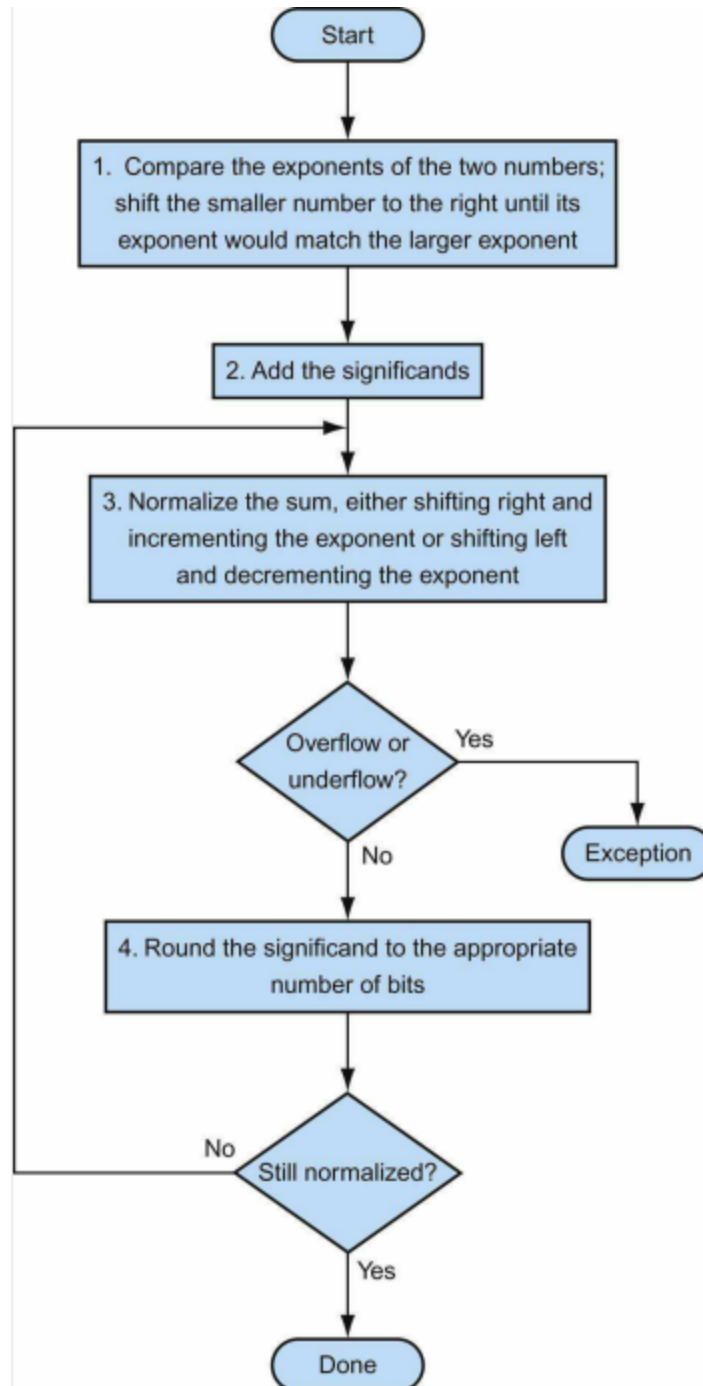


Figure 5: Floating-point addition and subtraction algorithm

## Multiplication algorithm

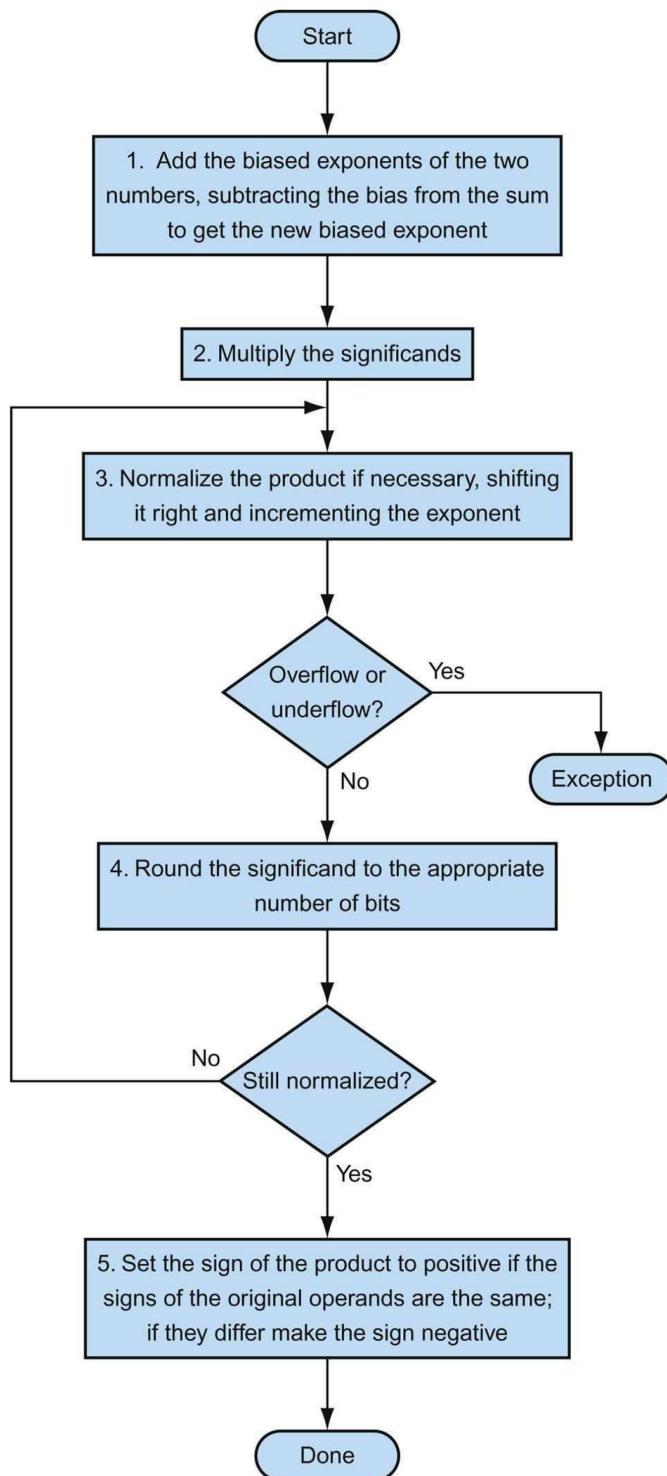


Figure 6: Floating-point multiplication algorithm